


Fog lights
(white & blue wires
tied together, cut at
IPDM connector E8,
wires 86 & 87)

Pico relay P/N 5593pt
40A NO/30A NC
88 Ohm coil (136mA)
has built-in quenching
resistor across coil

IPDM connector E8, wires 86 & 87
(white & blue wires tied together)
fog light power (output from IPDM)
On 12V
Off open

15A
Fuse

12V from battery

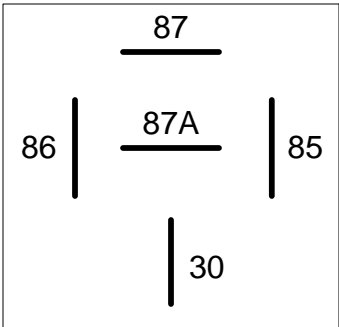

Pico relay connector layout
87 – NO, Normally Open relay connector
87A – NC, Normally Closed relay connector
86 – relay coil connector
85 – relay coil connector
30 – C, Common relay connector